

# Assignment 2

---

Sohan Sanjay Zense

CRS 2012

---


---

---




Q Design an adder subtractor 8 bit circuit using any 2-input gates and count the number of gates required & the delay of the circuit.

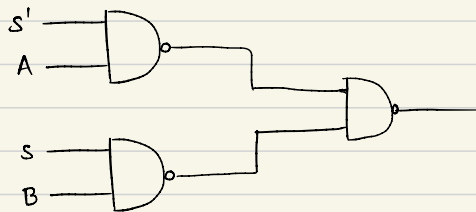The basic circuit of then the full circuit:




2x1 MUX

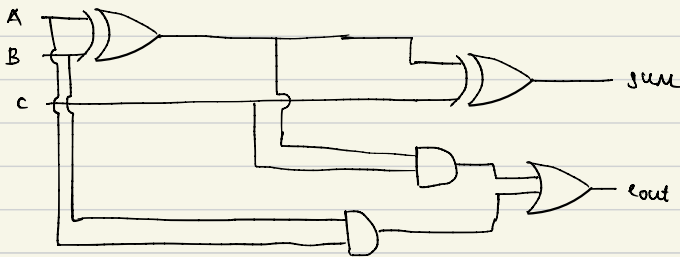

1-bit full adder

Number of gates in a 2x1 multiplexer = 3

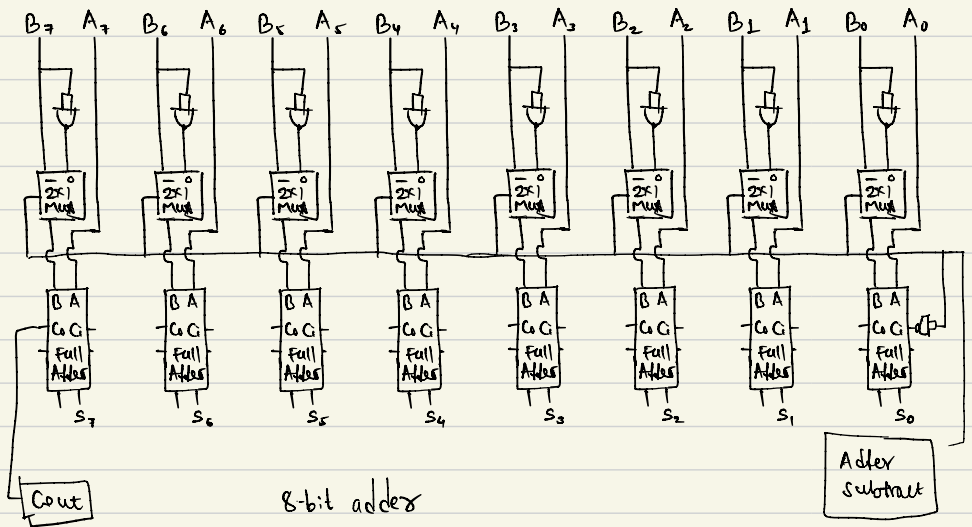Number of gates in a 1-bit full adder = 5



Total Number of Gates =  $9 + 8 \times 3 + 8 \times 5 = \underline{\underline{73}}$ .