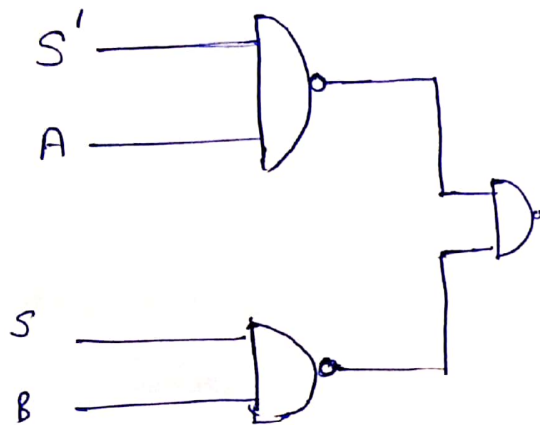


## Assignment-2

Q1 Design an odder subtractor 8 bit circuit using any 2-input gates, and count the number of gates required and the delay of the circuit.


### Solution

We first draw the basic circuit and then a full circuit.




Number of gates in  
a 2x1 MUX = 3.

2x1 MUX

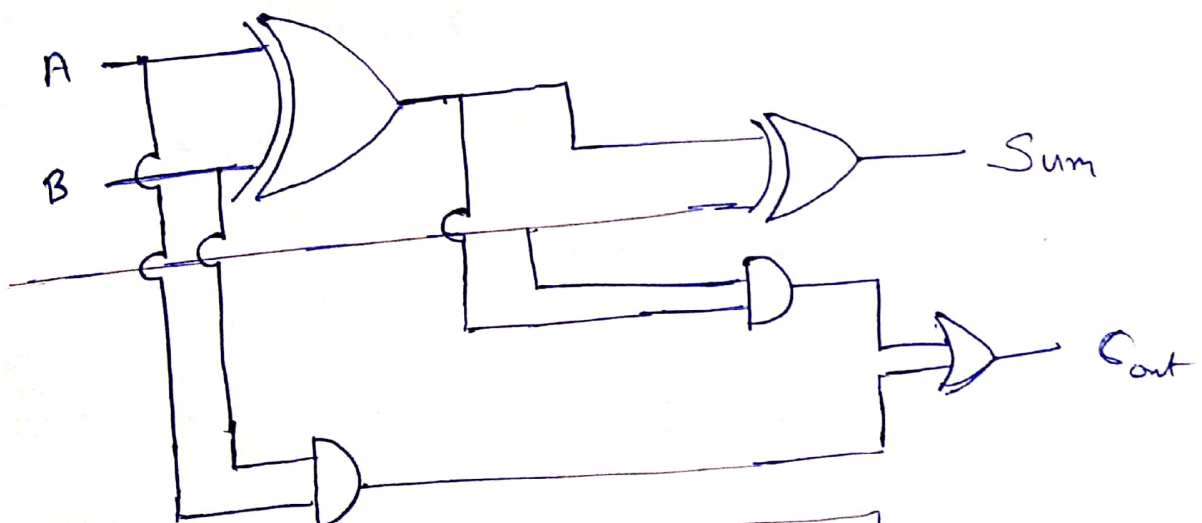

1-bit FULL ADDER

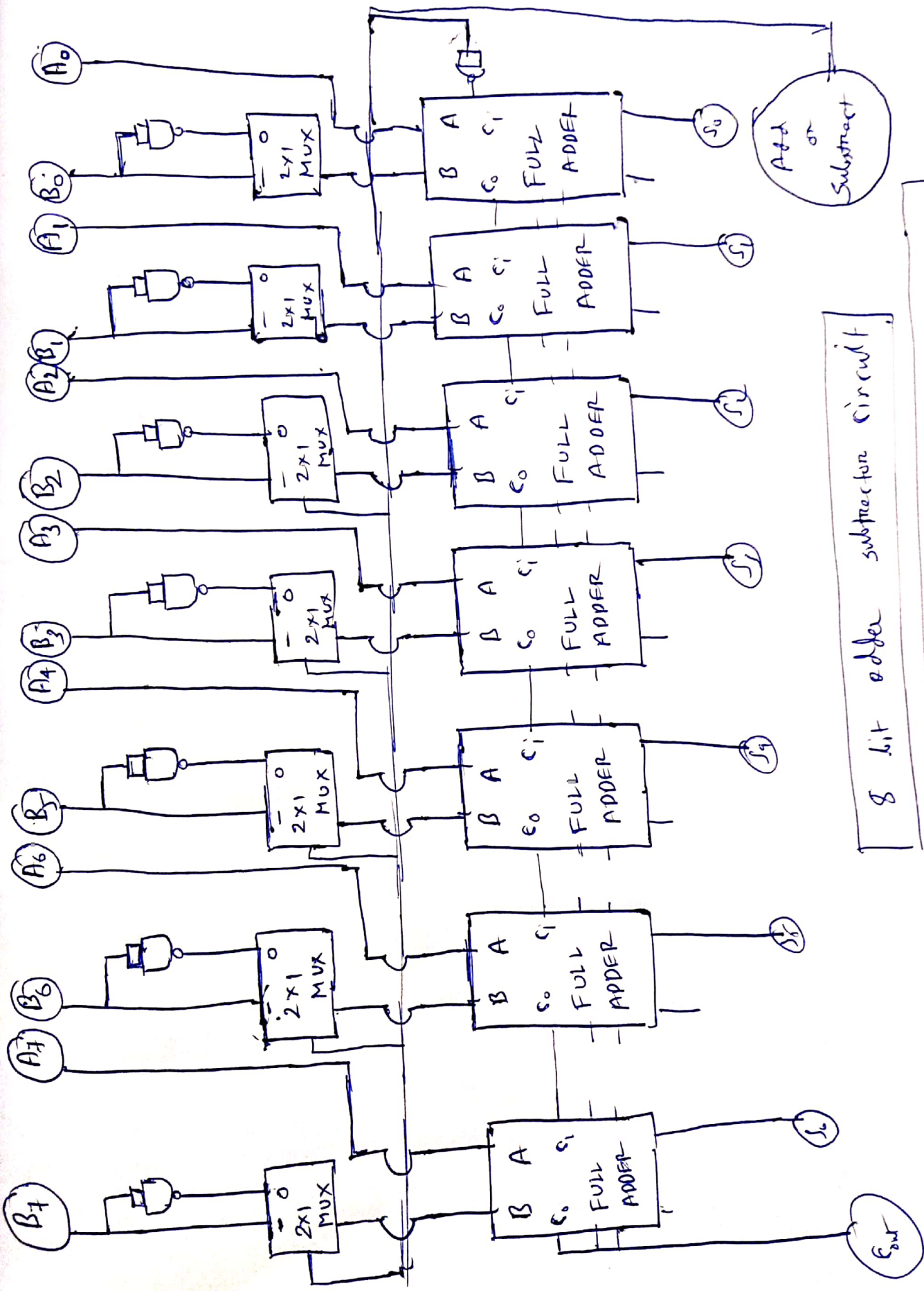Number of gates in a 1-bit Full ADDER = 5.



8 bit adder subtractor circuit

Total number of gates =  $9 + 8 \times 3 + 8 \times 5 = 73$