
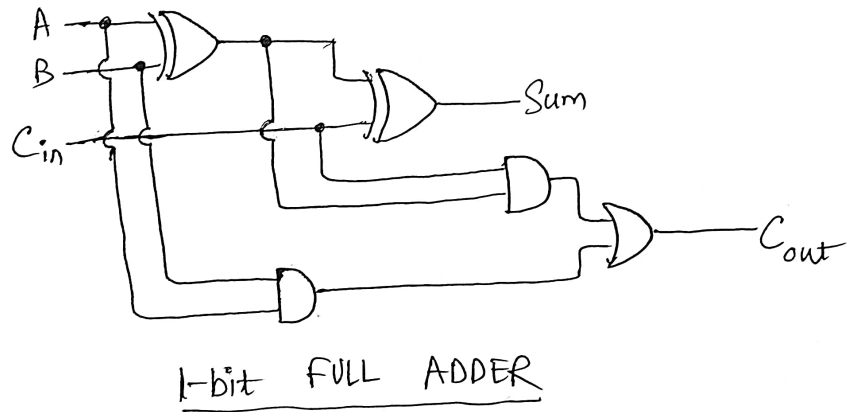


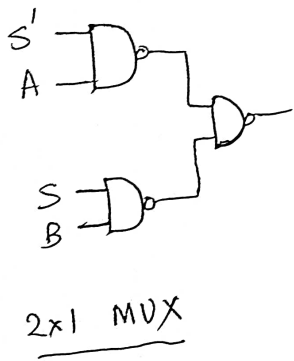- ① Design an adder-subtractor 8-bit circuit, using any 2-input gates, and count the number of gates required and the delay of the circuit (in 2's complement format)




No. of gates in a 2x1 MUX = 3

No. of gates in a 1-bit FULL ADDER = 5

Delay in a 2x1 MUX = 2td

Delay in a 1-bit FULL ADDER = 3td

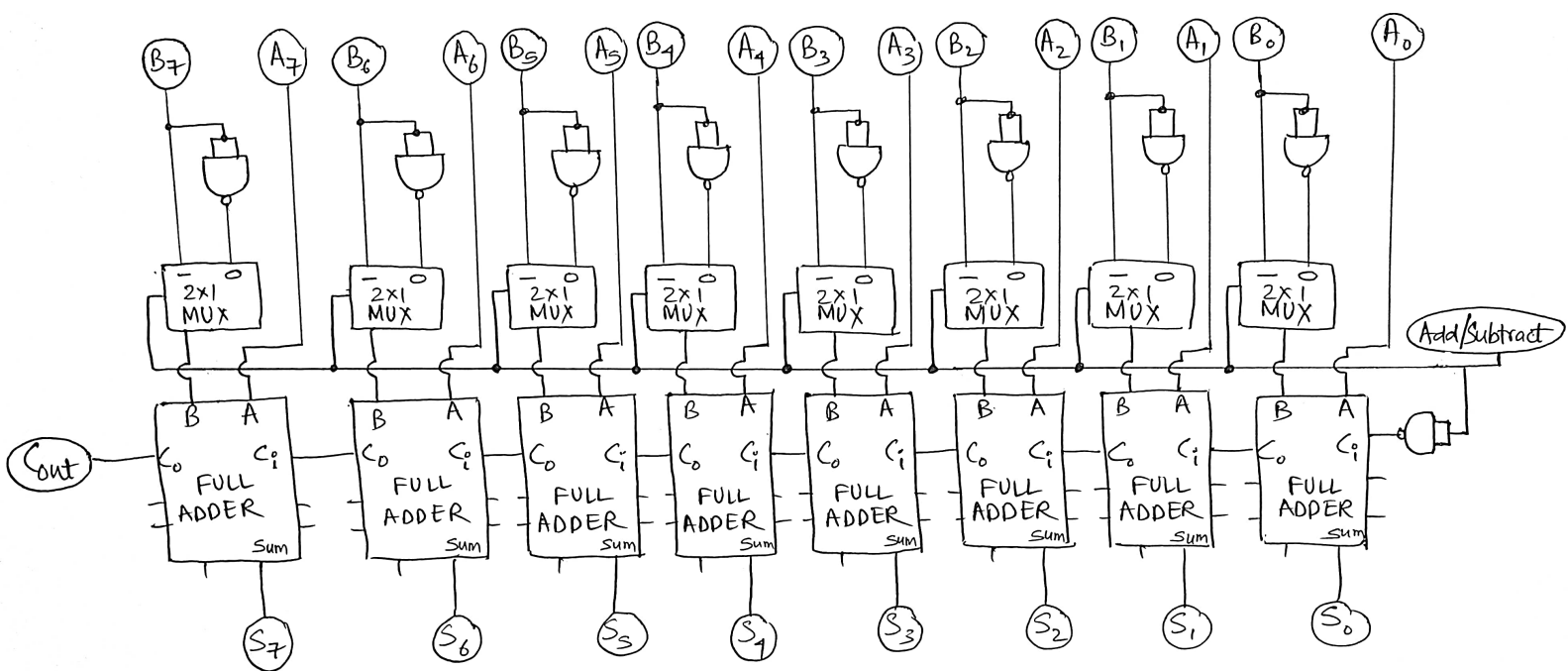


8-bit adder-subtractor circuit

$$\text{Total no. of gates} = 9 + 8(3) + 8(5) = 73$$

$$\text{Delay} = 3 + 8(3) = 27 \text{ td}$$


② Design a carry look-ahead 8-bit adder which outputs a 9-bit number. Check that the second method would be much faster.


Ans:

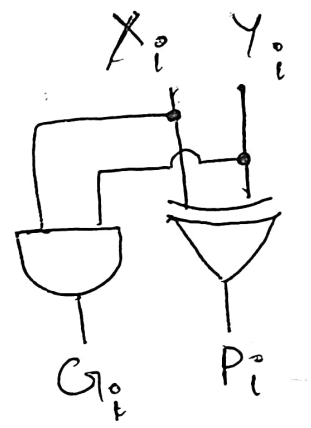

No. of gates in PG-Block = 2  
 Delay in PG-Block = 1td

PG - Block

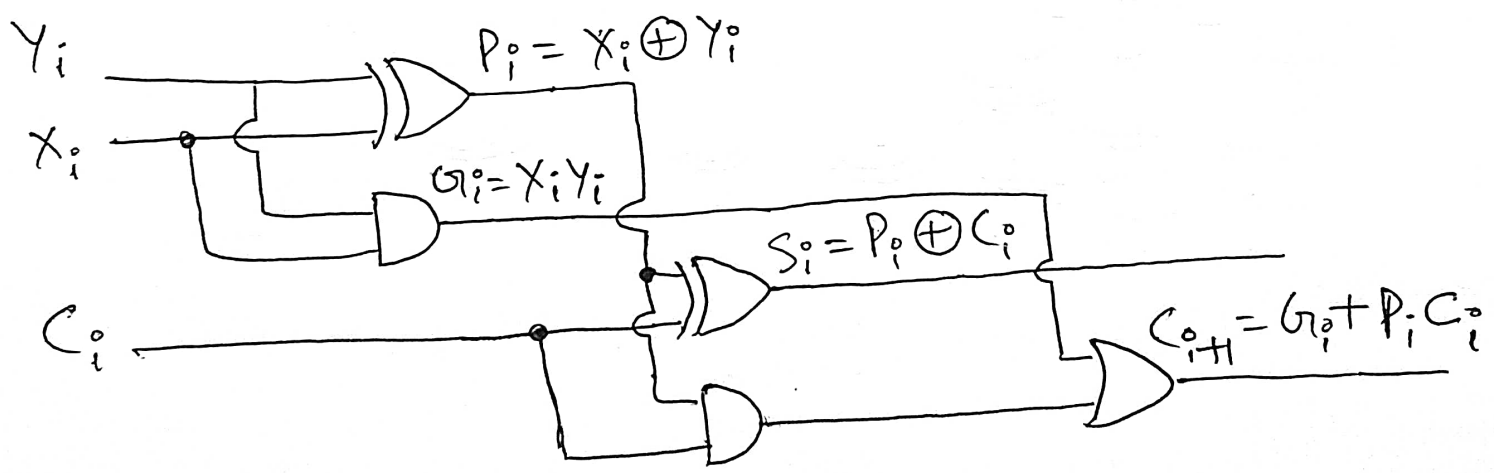

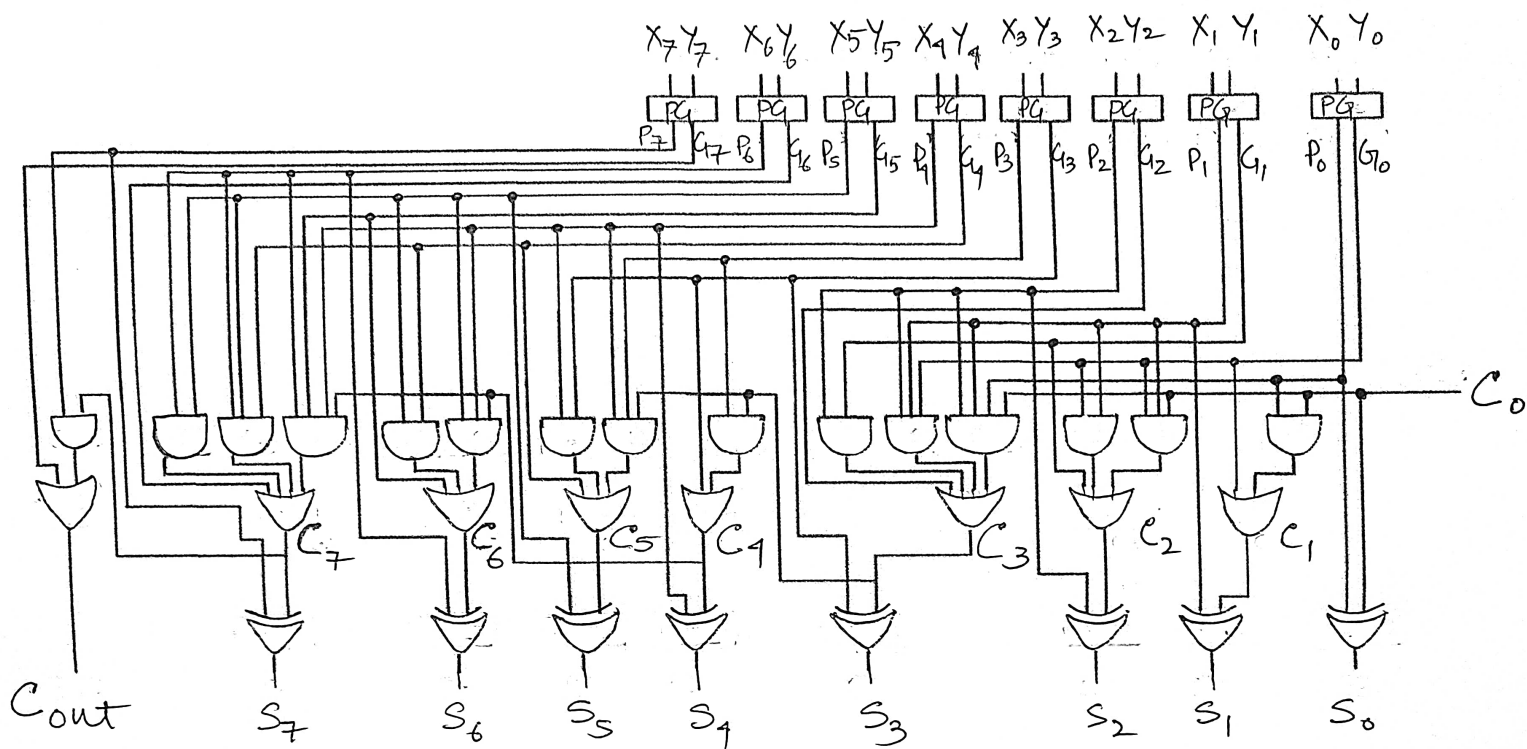


8-bit CLA.

Total no. of gates =  $8(2) + 15 + 8 + 8 = 47$

Delay = 4 td

Hence CLA is much faster.

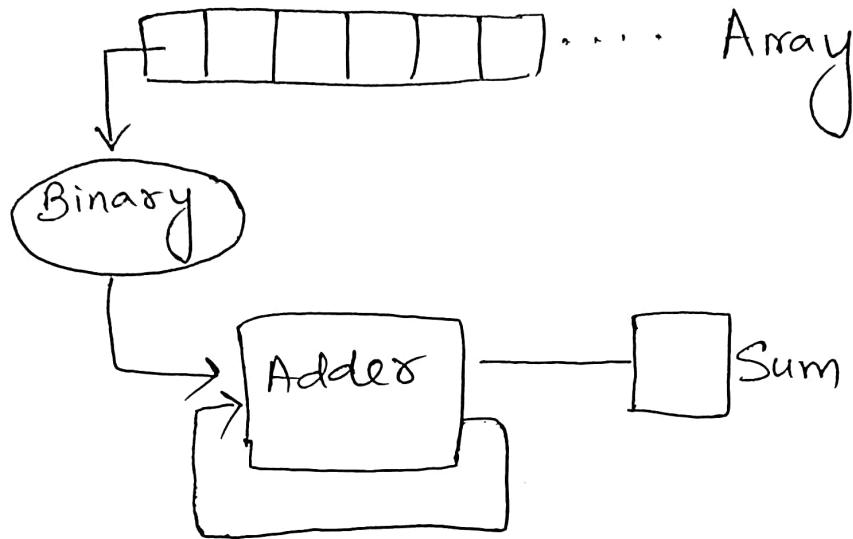③ Give the circuit idea for adding the values of all the elements of an array.



We first convert the array elements into 8-bit binary representation. Then we will <sup>take the</sup> 1st element of array & add it to  $0^8$  through 8-bit adder and  $S$  be the result. Then we will take the 2nd element of the array & add it to  $S$  through 8-bit adder and modify  $S$  to be the result. Like this we will continue. Finally  $S$  will have the sum of all the elements of the array.