

### Question:-

Design an adder-subtractor 8 bit circuit using only 2-input gates and Count the number of gates required and the delay of the circuit

Ans:- Our input bit number is 8

Now for 1st bit addition we only need only one half adder circuit - as there is no carry on the 1st bit addition.

2-bit addition gate calculation: (Half adder)

Let  $a_0, b_0$  be our input bit, Then let  $S_1$  be the Sum bit and  $C_1$  be the Carry bit.

$$\text{So, } S_1 = a_0 \oplus b_0 \text{ and } C_1 = a_0 b_0$$

$$\text{i.e., } S_1 = \cancel{a_0 b_0} + a_0 b_0' + a_0' b_0 \text{ and } C_1 = a_0 b_0$$

So for  $S_1$  we need  
2 AND GATE  
1 OR GATE  
and 2 NOT GATE

for  $C_1$  we need 1 AND gate.

So for a half adder we need  
2 NOT gate.  
3 AND gate.

2 bit addition with carry bit gate calculation:-

Let,  $a_1, b_1$  be two input bit and  $C_1$  be the carry bit then

$$S_2 = a_1 \oplus b_1 \oplus C_1 = a_1 b_1' C_1' + a_1' b_1 C_1' + a_1 b_1' C_1 + a_1 b_1 C_1$$

$$\text{and } C_2 = a_1 b_1 + a_1 C_1 + b_1 C_1$$

So required number of AND gate = 11  
OR gate = 5  
NOT gate = 3

So, for one full adder we need 11 AND gate & 5 OR gate.

Now for 8 bit addition we need one half adder and 7 full adder. Therefore total number of

$$\text{AND Gate} = 3 \times 1 + 7 \times 11 = 80$$

$$\text{OR gate} = 1 \times 1 + 7 \times 5 = 36$$

$$\text{NOT gate} = 2 \times 1 + 7 \times 3 = 22$$

Now for Substruction, we know that, in 2's Complement  $\bar{B} + 1 = -B$  So,  $A - B = A + \bar{B} + 1$

Therefore, Substruction of A & B is nothing the addition with initial carry 1

To perform Substruction for 8 bit number. We need 8 full adder and for calculation  $\bar{B}$  we need 8 more NOT gate.

So Total Number of required gate is

$$\text{AND gate is} = 8 \times 11 = 88$$

$$\text{OR Gate is} = 8 \times 5 = 40$$

$$\text{NOT gate is} = 8 \times 3 + 8 = 32$$

This is the Gate Calculation for Sequential logic Circuit.

For using Carry Look Ahead Adder (CLA) there are two functions one is generating function (G) and another is propagating function (P)

For  $i$ th bit


$$G_i = A_i B_i$$

$$P_i = A_i \oplus B_i$$


and  $C_i = A_i B_i + (A_i + B_i) C_{i-1} = G_i + P_i C_{i-1}$

So for 8 bit input we divide the block of size 2.

Now for one block

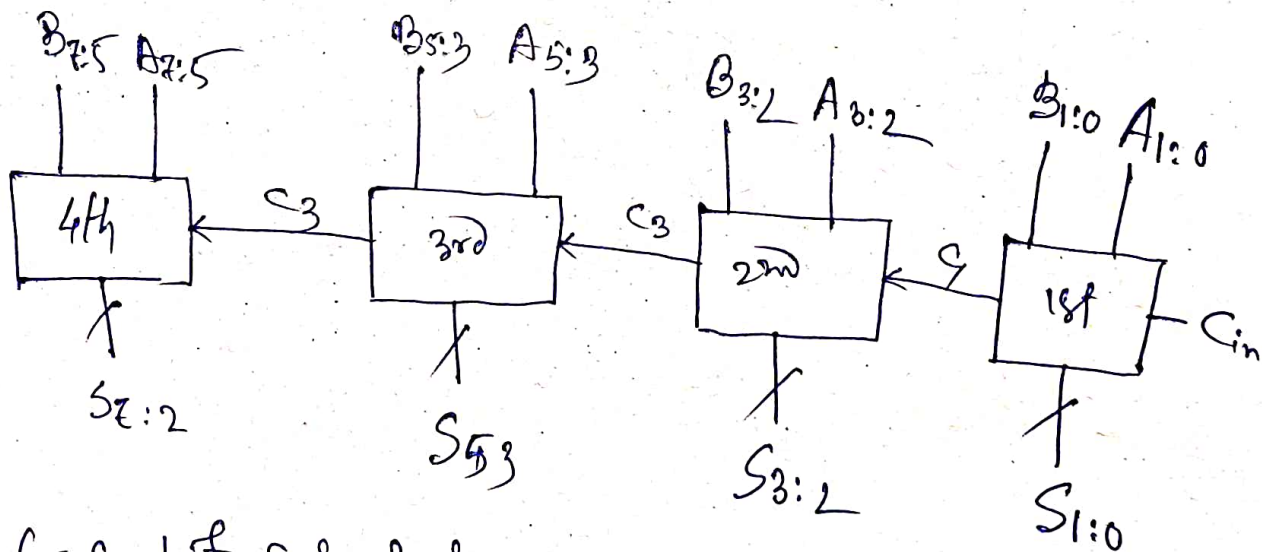

1st Block for sum bit calculation.

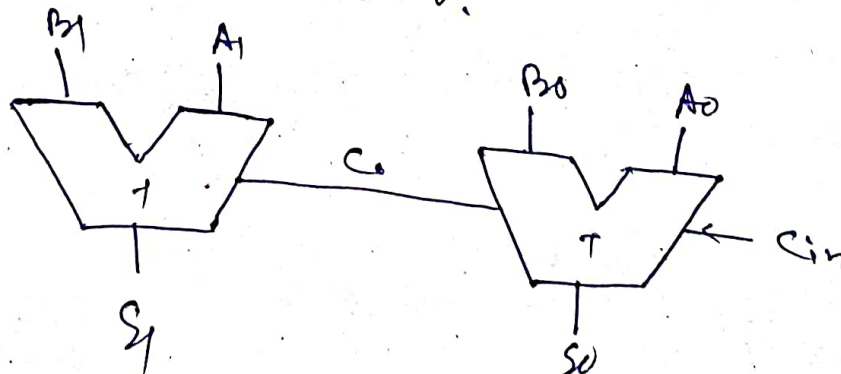




Now  $C = g_0 + P_0 \cdot C_{in}$

$$C = g_1 + P_1 \cdot C = g_1 + P_1 (g_0 + P_0 C_{in})$$

$$= (g_1 + P_1 g_0) + P_0 P_1 C_{in}$$

Where  $g_i = A_i B_i$  ,  $P_i = A_i \oplus B_i$

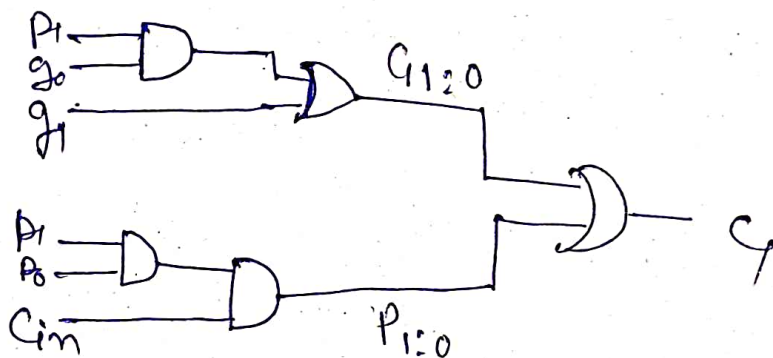If we know  $A_i, B_i$  Then we can easily calculate  $G_{1:0}$  and  $P_{1:0}$  and from these two we can find carry  
So, for the 1st block the carry bit the circuit is



~~So for each sum bit calculation we need two full adders and one block~~

So Total number of Gate ~~count~~ required for each block is

AND Gate =  $11 \times 2 + 3 = 25$

OR Gate =  $5 \times 2 + 2 = 12$

NOT Gate =  $3 \times 2 = 6$

So Total number is

AND Gate =  $25 \times 4 = 100$

OR Gate =  $12 \times 4 = 48$

NOT Gate =  $6 \times 4 = 24$

Comparison:-

So for using sequential adder circuit it takes  $O(n)$  times.

But for the 2<sup>nd</sup> part we need only  $O(\sqrt{n})$  times as we calculate this sum bit and carry bit for each block parallel.

Although the 2<sup>nd</sup> part we need more gates in counts but it is faster enough.