
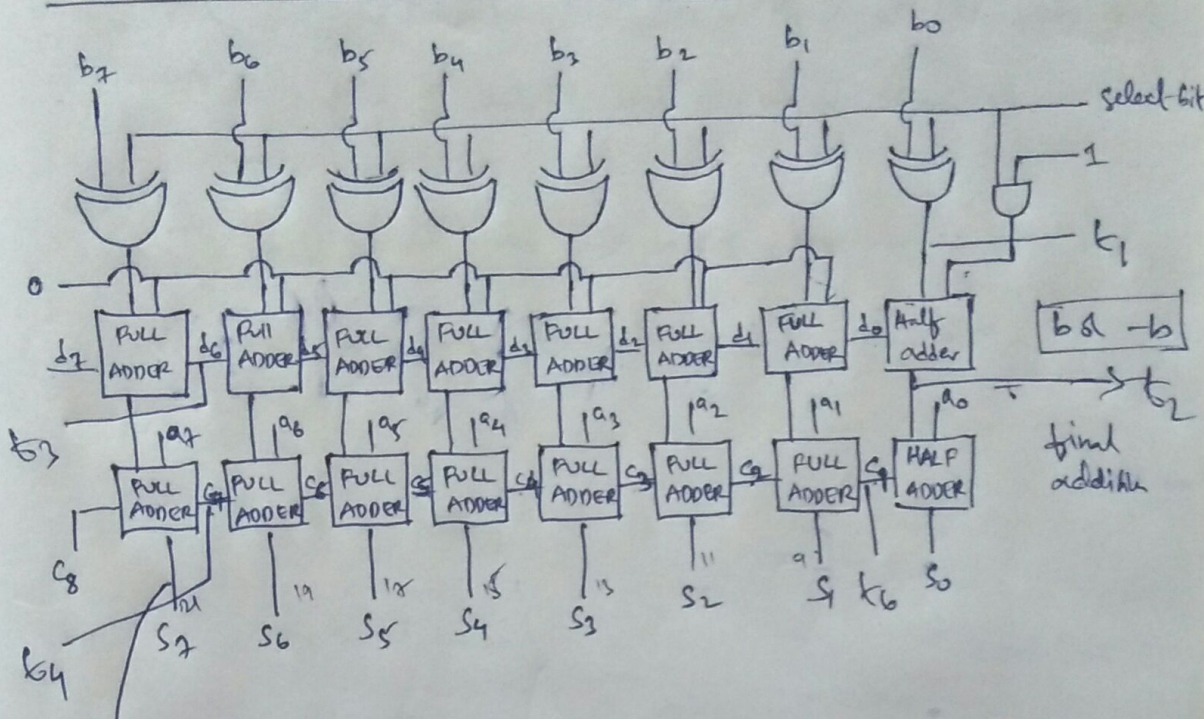



8-bit Adder-Subtractor Circuit

 


Half ADDER



Full ADDER .

 

XOR

 

Circuit Complexity:

38 - XOR gates , 31 - AND gates , treating XOR as 2-input gate .

otherwise .

$(38 \times 2) + 31$ - AND gates and 38 - OR gates

so 107 - AND gates and 38 - OR gates .

Time Delay: (Assume unit time for AND gate and OR gate).

So an Half adder takes 2 units of time to ^{output} carry bit and 2 units of time to output sum bit.

While
For a Full adder takes 2 units of time to output carry bit and 4 units of time to output sum bit.

So total time delay

$$t_1 = 2 \text{ units.}$$

$$t_2 = (2+2) = 4 \text{ units.}$$

$$t_3 = 15 \text{ units.}$$

~~$$t_4 = 12 \text{ units.}$$~~

$$t_6 = 5 \text{ units.}$$

$$t_4 = 12 \text{ units}$$

$$t_5 = 21 \text{ units.}$$

So total time will be equal to $t_5 = 21 \text{ units.}$

3. Give the circuit idea for adding all the elements of an array.

/* sum of elements of an array */

```
int i;
```

```
int A[3] = {a1, a2, a3};
```

```
int sum = 0;
```

```
for (i = 0; i < 3; ++i) {
```

```
    sum = sum + A[i];
```

```
}
```

MIPS code:

\$s0 = i, \$s1 = base address of A, \$s2 = sum

addi \$s2, \$0, 0 # sum = 0.

addi \$t0, \$0, 0 # i = 0.

addi \$t0, \$0, 3 # \$t0 = 3

loop:
slt \$t1, \$s0, \$t0 # if (i < 3) \$t1 = 1, else \$t1 = 0.

bgez \$t1, \$0, done # if \$t1 = 0, branch done.

lw \$t2, (\$s1)

add \$s2, \$s2, \$t2


addi \$s1, \$s1, 4

addi \$s0, \$s0, 1


j loop

done:


addi \$s2, \$0, 0

 

addi \$s0, \$0, 0

 


addi \$t0, \$0, 3

 


loop:


slt \$t1, \$s0, \$t0

 


bge \$t1, \$0, done

 


lw \$t2, (\$s0)

 


add \$s2, \$s2, \$t2

 


addi \$sp, \$sp, 4

 

addi \$s0, \$s0, 2

 

j loop

 

Now again repeat loop. 2 was found, until bge, when \$t1 = 0, that fails to the address done.

slt \$t1, \$s0, \$t0

